

ElecEng 2CF4

Assignment 4 Report 2


Joshua Obljubek-Thomas

400506256

EXERCISE #2: TRANSIENT 2ND DEGREE CIRCUIT

Joshua Oblubek-Thomas, 400506256

1. Circuit Schematic;

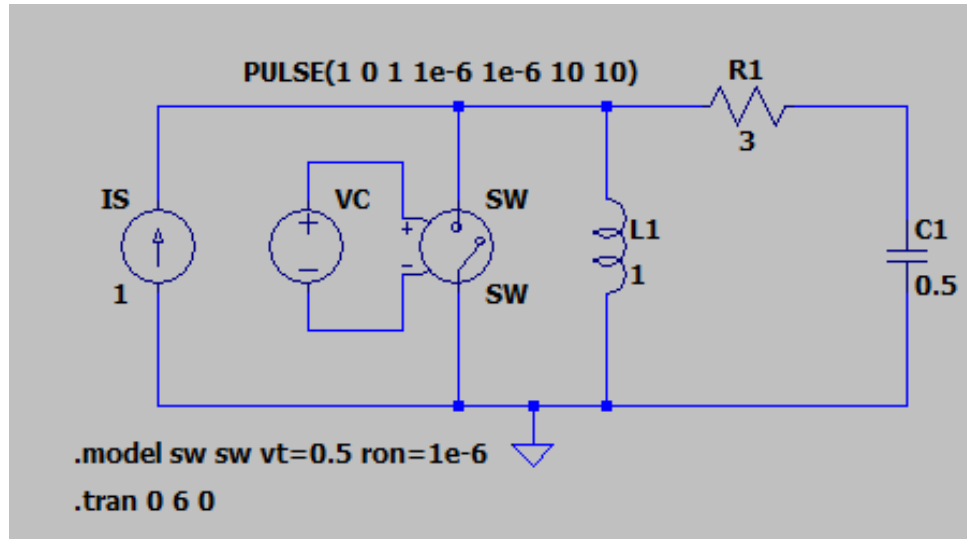

2. Spice netlist

* C:\Users\Josh\Documents\COMPENG\Y2S2\2CF3\Assignment4\Q2.asc

IS 0 N001 1

VC N003 N004 PULSE(1 0 1 1e-6 1e-6 10 10)

R1 N002 N001 3

C1 N002 0 0.5

SW 0 N001 N003 N004 SW

L1 N001 0 1


.model sw sw vt=0.5 ron=1e-6

.tran 0 6 0

.backanno

.end

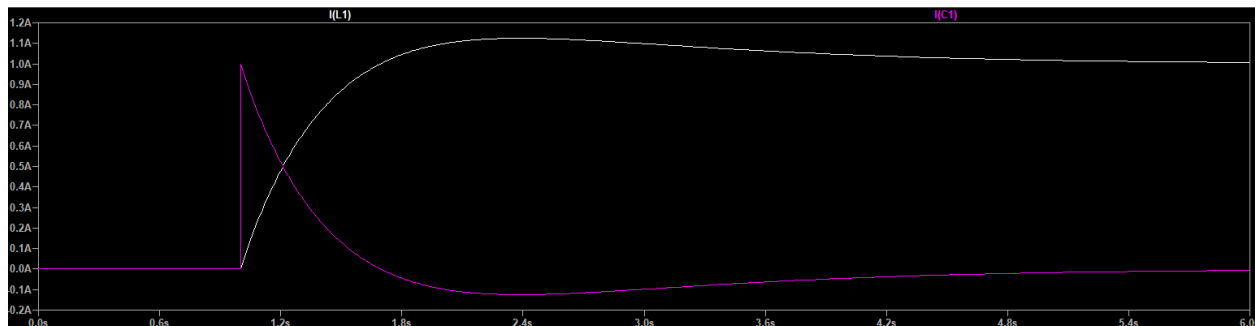3. Plot of $i_L(t)$ and $i_C(t)$ from the LTspice simulation.



4. Analytical solution for $i_L(t)$ and $i_C(t)$ based on the Laplace transform

Initial Conditions:

Capacitor Open circuit and Inductor short circuit


$$I_{L,0-} = 0A$$

$$I_{C,0} = 0V$$

Redrawing the circuit:

$$i_C(t) = C \frac{dv_C(t)}{dt} \leftrightarrow I_C(s) = sCV_C(s) - Cv_C(0_-)$$
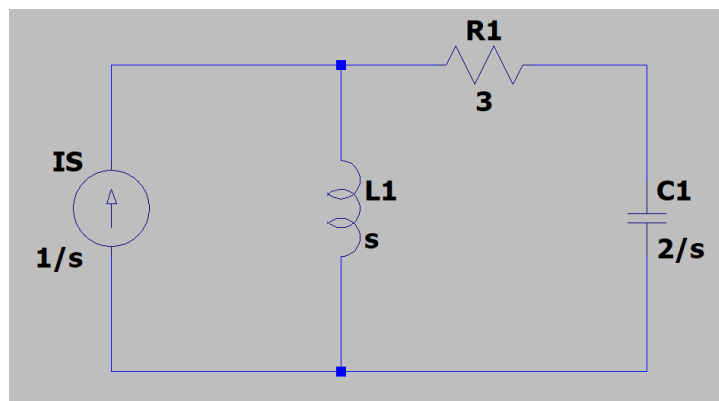
$$v_L(t) = L \frac{di_L(t)}{dt} \leftrightarrow V_L(s) = sLI_L(s) - Li_L(0_-)$$



I_L found with current division:

$$I_L(s) = \frac{1}{s} \left[\frac{R + \frac{2}{s}}{s + R + \frac{2}{s}} \right]$$

$$L^{-1}\{I_L(s)\}$$

$$= \frac{1}{s} \left[\frac{3 + \frac{2}{s}}{s + 3 + \frac{2}{s}} \right]$$

$$L^{-1} \left\{ \frac{3 + \frac{2}{s}}{s + 3 + \frac{2}{s}} \right\} = 1 + e^{-t} - 2e^{-2t}$$

I_C found with current division:

$$I_C(s) = \frac{1}{s} \left[\frac{s}{R + \frac{s}{2} + s} \right]$$

$$= \frac{1}{s} \left[\frac{s}{3 + \frac{s}{2} + s} \right]$$

$$L^{-1}\{I_C(s)\}$$

$$= -e^{-t} + 2e^{-2t}$$


Summary

$$I_L(t) = 1 + e^{-t} - 2e^{-2t}$$

$$I_C(t) = -e^{-t} + 2e^{-2t}$$

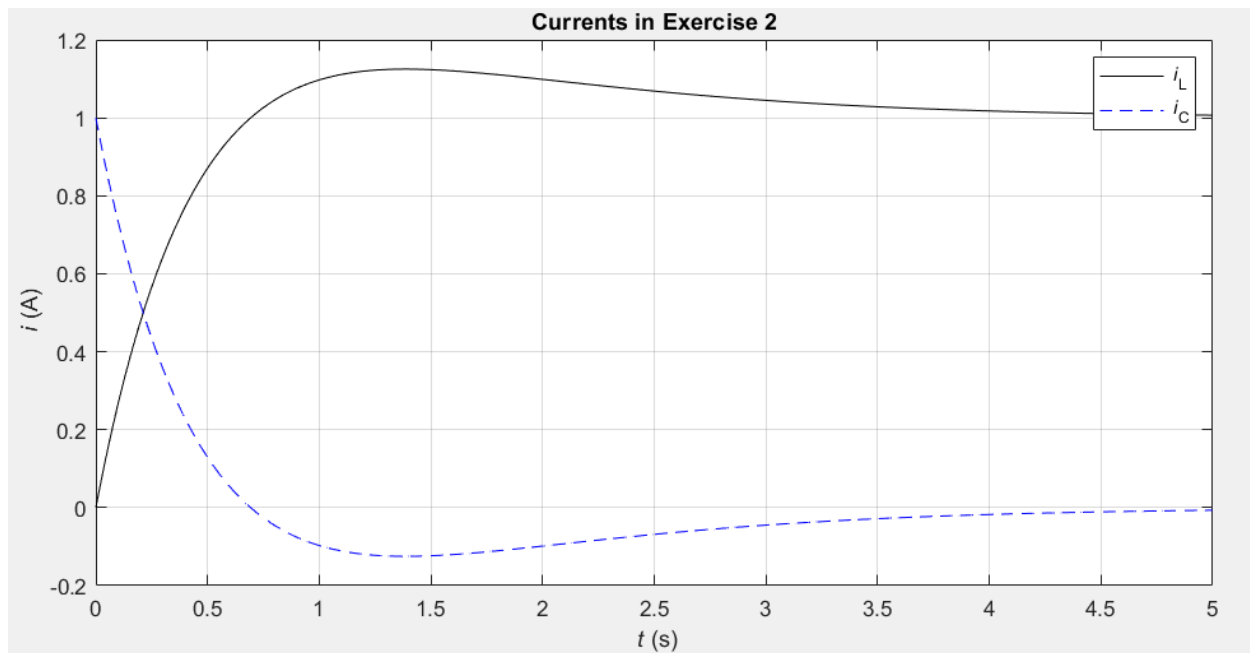5. MATLAB source code and plot

```
clear all; close all;  
t = linspace(0, 5, 1001); % vector of 1001 time samples from 0 to 5 s  
iL = 1+exp(-t)-2*exp(-2*t); % change this to the function iL(t) you found from Laplace analysis  
iC = 2*exp(-2*t)-exp(-t); % change this to the function iC(t) you found from Laplace analysis  
figure;  
plot(t, iL, '-k') % plot curve in solid black line  
hold on;  
plot(t, iC, '--b') % plot curve in dash blue line  
hold off;  
grid on;  
legend('iL', 'iC')  
title('Currents in Exercise 2')  
xlabel('t (s)');  
ylabel('i (A)');
```



6. Does the LTspice simulation agree with the MATLAB plot of the theoretical results? Justify your answer.

The LTspice and MATLAB plots of $I_L(t)$ and $I_C(t)$ show the expected damped transient response of a second-order system. Features observed:

- Distinct time constants: Both simulations capture the fast and slow decay components in the currents
- Overshoot and settling behavior: The curves transition smoothly towards steady-state values
- Phase relationship: LTspice confirms that $I_C(t)$ and $I_L(t)$ follow the expected inverse relationship