

ElecEng 2CF4


Assignment 3 Report 1

Joshua Obljubek-Thomas

400506256

EXERCISE #1: RLC SERIES NETWORK AT RESONANCE

1. Schematic

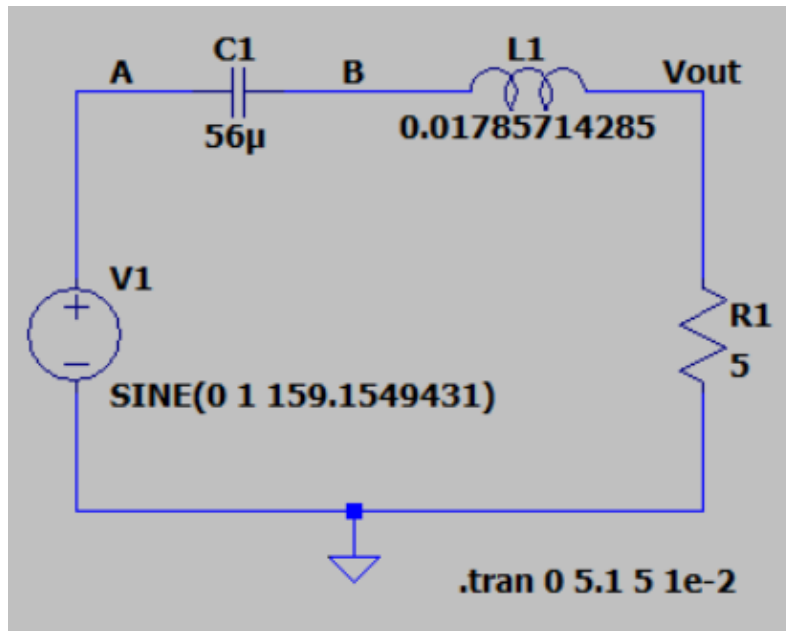

2. Spice Netlist

```
* C:\Users\Josh\Documents\COMPENG\Y2S2\2CF3\Assignment3\q1.asc
V1 A 0 SINE(0 1 159.1549431)
C1 B A 56μ
L1 B Vout 0.01785714285
R1 Vout 0 5
.tran 0 5.1 5 1e-2
.backanno
.end
```

3. Calculations for R, C, L, Q, f_0 , and the phasors V_L and V_C

Calculating for R:

When in resonance, $Z_C + Z_L = 0$, thus, $Z(W_0) = Z_R = R = 5\Omega$

Calculating for C:

Student #: 400506256

Calculating for L:

$$W_0 = \frac{1}{\sqrt{LC}}$$

$$1000 = \frac{1}{L(56\mu F)}$$

$$L = \frac{1}{56} H = 0.01785714285 H$$

Calculating for Q:

$$Q = \frac{W_0 L}{R}$$

$$Q = \frac{1000 \times \left(\frac{1}{56}\right)}{5}$$

$$Q = 3.57142857143$$

Calculating for V_L and V_C :

$$X_C = \frac{1}{\omega C} = 17.857$$

$$X_L = \omega L = 17.857$$

$$I = \frac{1\angle 0^\circ}{5} = 0.2\angle 0^\circ \text{ A}$$

$$V_L = 17.857 \times (0.2\angle 0^\circ \text{ A}) = 3.571428572$$


- Inductor voltage leads current by 90°

$$- V_L = 3.57\angle 90^\circ \text{ V}$$

$$V_C = 17.857 \times (0.2\angle 0^\circ \text{ A}) = 3.571428572$$

- Capacitor voltage lags current by 90°

$$- V_C = 3.57\angle -90^\circ \text{ V}$$

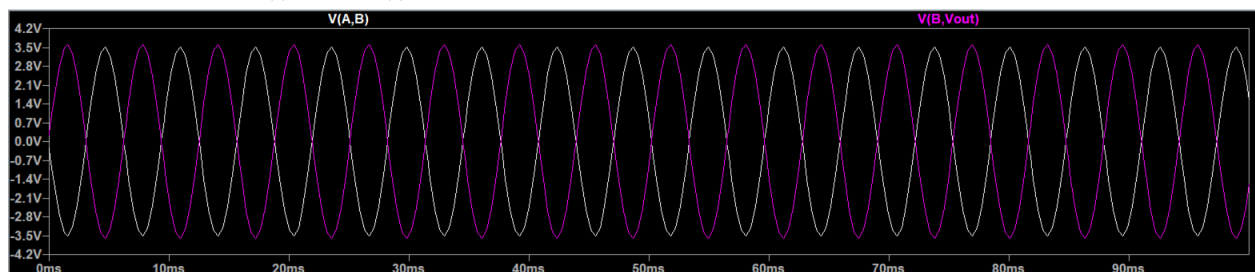
4. Plot of the $v_C(t)$ and $v_L(t)$ waveforms from the simulation

5. Do the simulation results for $v_C(t)$ and $v_L(t)$ at the resonant frequency confirm the magnitude and phase calculation for the phasors V_L and V_C in part 4? Justify your answer.

The simulation matches the two voltage phasors $V_C = 3.57\angle -90^\circ \text{ V}$ and $V_L = 3.57\angle 90^\circ \text{ V}$. It can be seen that the amplitude of the voltage reaches 3.57V and the two waveforms are 180 degrees out of phase.

EXERCISE #2: RLC SERIES NETWORK AS A BANDPASS FILTER

1. Schematic

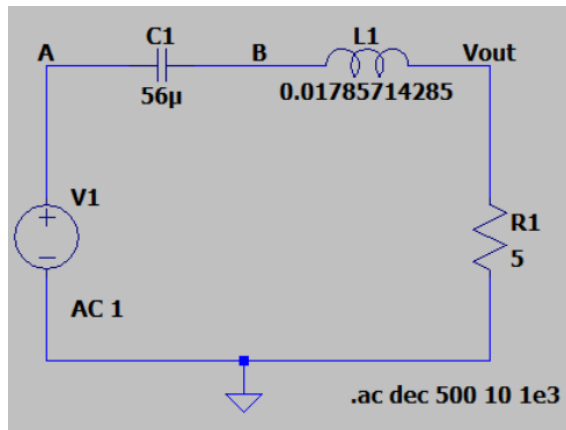

2. Spice Netlist

```
* C:\Users\Josh\Documents\COMPENG\Y2S2\2CF3\Assignment3\q2.asc
V1 A 0 AC 1
C1 B A 56μ
L1 B Vout 0.01785714285
R1 Vout 0 5
.ac dec 500 10 1e3
.backanno
.end
```

3. Calculation of the 3-dB BW, f_{LO} and f_{HI}

$$Q = 3.57142857143$$

$$\omega_0 = 1000 \text{ rad/s}$$

$$\omega_{LO} = \omega_0 \left[-\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$

$$\omega_{LO} = 869.7524449 \text{ rad/s}$$

$$f_{LO} = 138.425 \text{ Hz}$$


$$\omega_{HI} = \omega_0 \left[\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$

$$\omega_{HI} = 1149.752445 \text{ rad/s}$$


$$f_{HI} = 182.989 \text{ Hz}$$

$$BW = f_{HI} - f_{LO} = 44.563 \text{ Hz}$$

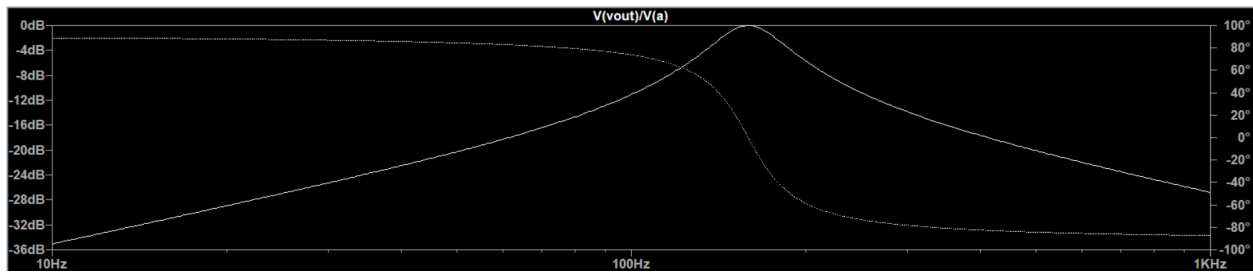4. Magnitude (in dB) and phase (in degrees) plot of G_v versus frequency from the simulation



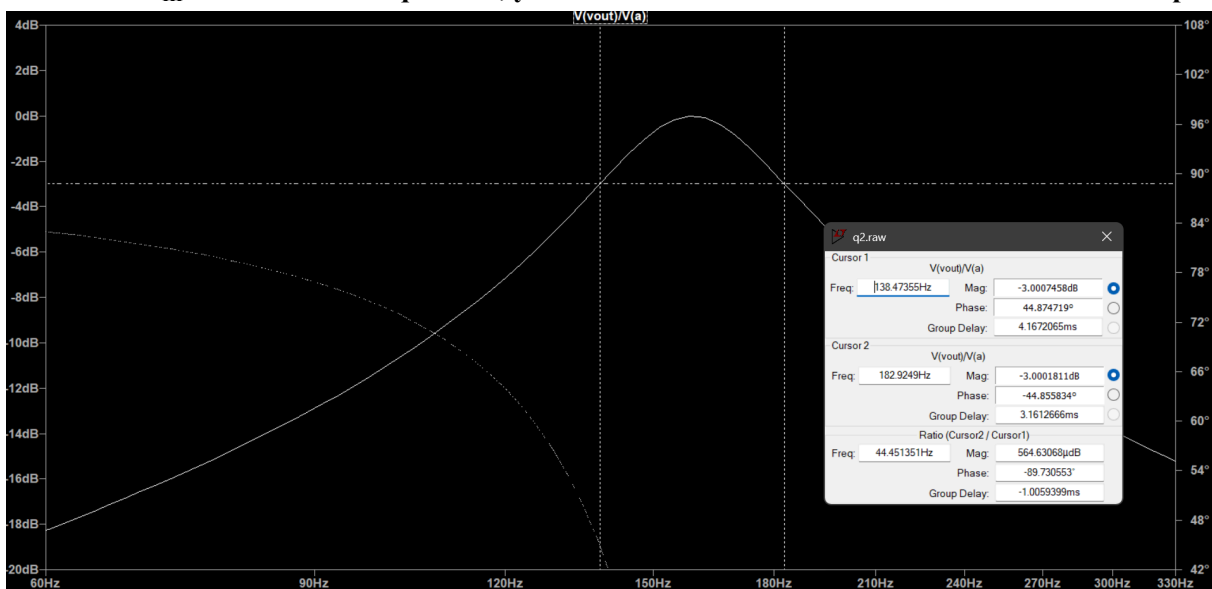5. Does the magnitude-dB plot of vG versus frequency confirm your calculations for BW, f_{LO} , and f_{HI} ? To answer this question, you need to read the values of LOF and HIF from the plot.



The cursors on the graph above show that the calculated values of 138.4Hz and 182.8Hz correspond to the 3dB frequency cutoffs.

6. What are the values of the phase of vG at the resonant frequency f_0 as well as the cut-off frequencies, f_{LO} and f_{HI} , according to the simulation plot? What are these values according to theory? Is there an agreement?

Phase at f_{Res} : 47.257mdeg = 0deg

Phase at f_{LO} : 44.87deg = 45deg

Phase at f_{HI} : -44.85deg = -45deg

The voltage gain $VG(j\omega) = \frac{V_{out}}{V_s}$ where V_{out} is taken across the resistor R . In a series RLC circuit, the total impedance is $Z_{total} = R + j(\omega L - \frac{1}{\omega C})$ and the voltage across the resistor is

$VR = IR = \frac{V_s R}{Z_{total}}$. The phase shift out of the output voltage $V_G(j\omega)$ depends on the reactance. When $X_L > X_C$ (inductive dominance), the circuit behaves inductively, and the current lags voltage. When $X_C >$

X_L (capacitive dominance), the circuit behaves capacitively, and the current leads the voltage. At resonance (ω_0), $X_L = X_C$, meaning the impedance is purely resistive, and there is no phase shift (0deg).

At f_{LO} (lower cutoff frequency):

- The circuit is still capacitive ($X_C > X_L$), meaning the output voltage lags the input current and the phase shift is +45deg

At f_{HI} (higher cutoff frequency):

- The circuit becomes inductive ($X_L > X_C$), meaning the output voltage leads the input current and the phase shift is -45deg


At resonance:

- $X_L = X_C$ and the phase shift is 0deg

Thus, the values are in agreement with the observations from the simulation.

EXERCISE #3: LOW-PASS FILTER

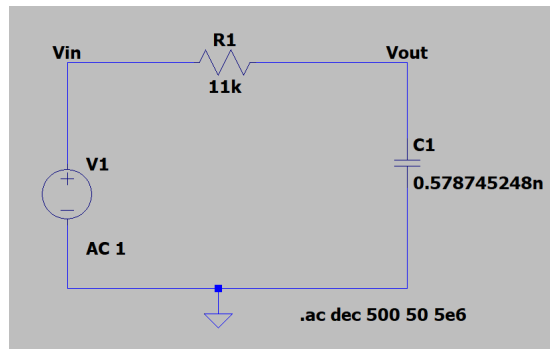1. Include the complete schematic (screenshot or image export).



2. Include the complete netlist (View→SPICE Netlist).

```
* C:\Users\Josh\Documents\COMPENG\Y2S2\2CF3\Assignment3\q3.asc
V1 Vin 0 AC 1
R1 Vout Vin 11k
C1 Vout 0 0.578745248n
.ac dec 500 50 5e6
.backanno
.end
```

3. Include the values of R and C. Show the calculation for C.

$$R = 11k$$


$$W_0 = \frac{1}{RC}$$

$$C = \frac{1}{2\pi f_0 R}$$


$$C = 5.78745248 \times 10^{-10} \text{ F}$$

$$C = 0.578745248 \text{ nF}$$

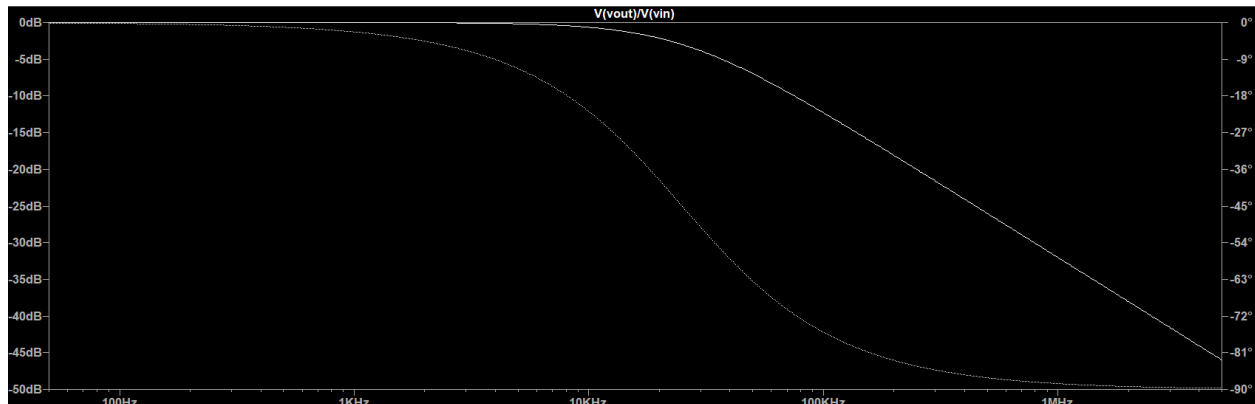4. Include the magnitude-dB plot of the transfer function obtained from the simulation.



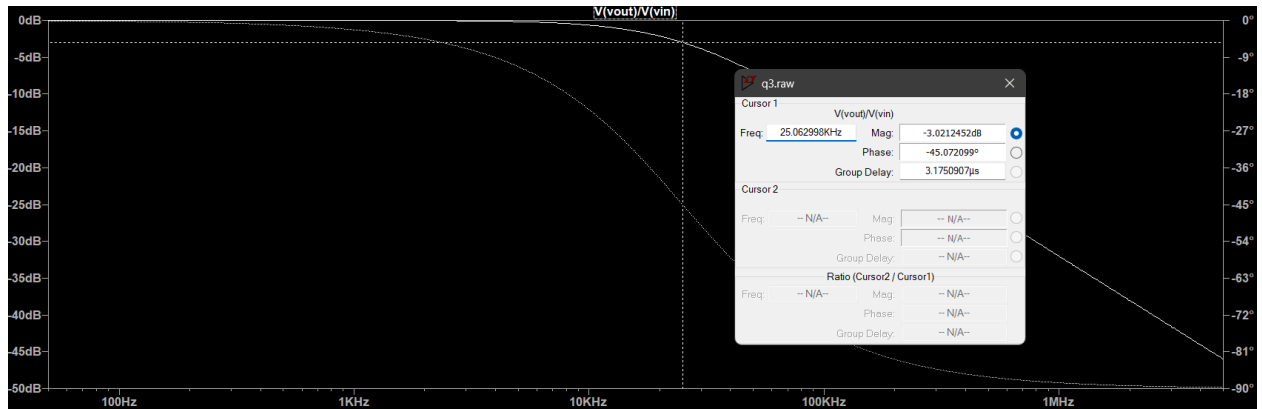
5. From the magnitude-dB plot of the transfer function, determine the cut-off frequency. Is it in agreement with the required value of 25 kHz?



As seen by the cursor placed at the 3dB cutoff frequency, the filter is in agreement with the required value of 25 kHz.

EXERCISE #4: HIGH-PASS FILTER

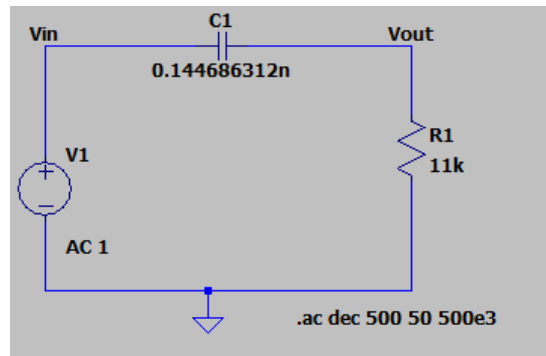1. Include the complete schematic (screenshot or image export).



2. Include the complete netlist (View→SPICE Netlist).

```
* C:\Users\Josh\Documents\COMPENG\Y2S2\2CF3\Assignment3\q4.asc
V1 Vin 0 AC 1
R1 Vout 0 11k
C1 Vout Vin 0.144686312n
.ac dec 500 50 500e3
.backanno
.end
```

3. Include the values of R and C. Show the calculation for C.

$$R = 11k$$


$$W_0 = \frac{1}{RC}$$

$$C = \frac{1}{2\pi f_0 R}$$


$$C = 1.44686312 \times 10^{-10} \text{ F}$$

$$C = 0.144686312 \text{ nF}$$

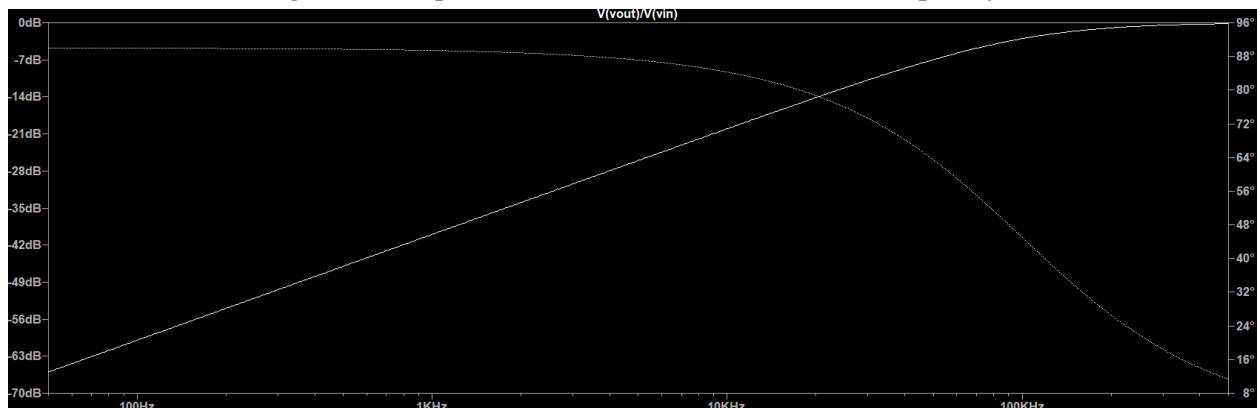4. Include the magnitude-dB plot of the transfer function versus frequency.



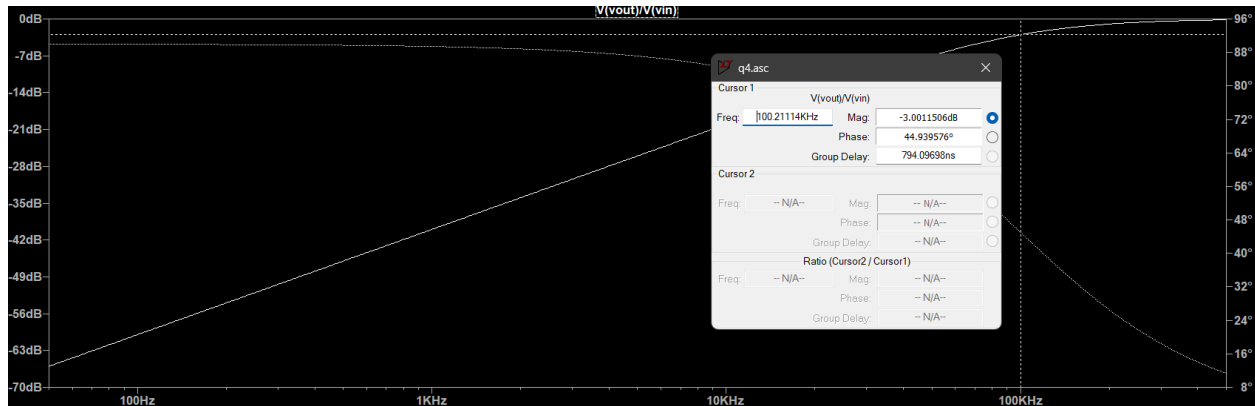5. From the magnitude-dB plot of the transfer function, determine the cut-off frequency. Is it in agreement with the required value of 100 kHz?



As seen by the cursor placed at the 3dB cutoff frequency, the filter is in agreement with the required value of 100 kHz.