

# ElecEng 2CF4


## Assignment 1 Report 2

Joshua Obljubek-Thomas

400506256

## 2.A.

### 1. Image of Schematic

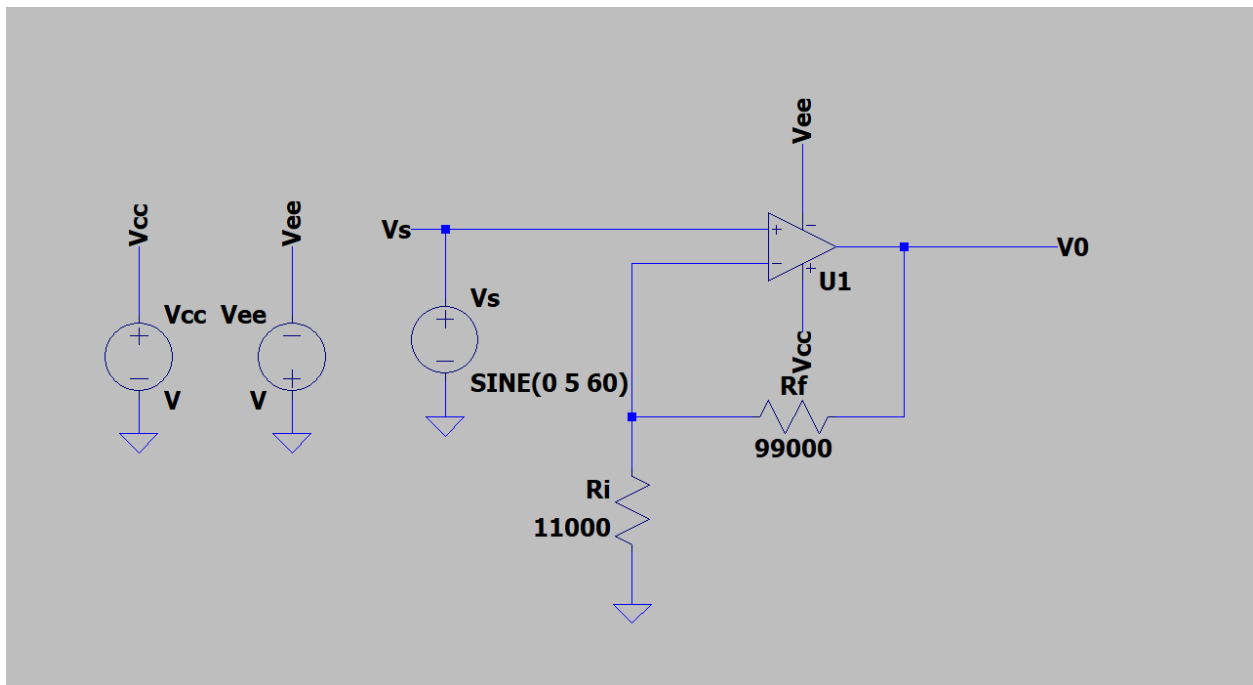


### 2. Spice Netlist

```
* C:\Users\Josh\Documents\COMPENG\Y2S2\2CF3\Assignment1\Q2.asc
Rf V0 N001 99000
Ri 0 N001 11000
X$U1 Vs N001 Vcc Vee V0 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m Rail=0
Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vcc Vcc 0 V
Vee 0 Vee V
Vs Vs 0 SINE(0 5 60)
.lib UniversalOpAmp2.lib
.backanno
.end
```

## 2.B.
 
### 1. Plot of $V_o$ and $V_s$ as a function of time



### 2. Spice Netlist

```
* C:\Users\Josh\Documents\COMPENG\Y2S2\2CF3\Assignment1\Q2.asc
Rf V0 N001 99000
Ri 0 N001 11000
X$U1 Vs N001 Vcc Vee V0 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m Rail=0
Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vcc Vcc 0 100
Vee 0 Vee 0
Vs Vs 0 SINE(0 5 60)
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

### 3. State whether your circuit achieved the desired gain of 10


The circuit achieved the desired gain of 10. However, the limits of the power supplies cause for the output to be clipped due to saturation.

### 4. State whether it is operating in a nonlinear regime. Justify your statement.

The circuit is operating in a nonlinear way because  $V_o$  doesn't fully follow the  $V_s$  during the negative half-cycles. This happens because the negative terminal of the op-amp is 0, so it can't produce negative voltages due to saturation. While the positive half-cycles are amplified as expected with a gain of 10, the negative half-cycles are cut off at 0 V, leading to clipping and nonlinearity.

## 2.C.
 
### 1. Plot of $V_o$ and $V_s$ as a function of time



### 2. Spice Netlist

```
* C:\Users\Josh\Documents\COMPENG\Y2S2\2CF3\Assignment1\Q2.asc
Rf V0 N001 99000
Ri 0 N001 11000
X$U1 Vs N001 Vcc Vee V0 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m Rail=0
Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vcc Vcc 0 100
Vee 0 Vee 100
Vs Vs 0 SINE(0 5 60)
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

### 3. State whether your circuit achieved the desired gain of 10.


The circuit achieves the gain of 10 at all times.

### 4. State whether it is operating in a linear or a nonlinear regime. Justify your statement.

The circuit operates in a linear regime because  $V_o$  follows  $V_s$  with the correct gain of 10 for both positive and negative cycles. The two power rails being set at +100 and -100 provide enough range for the op-amp to amplify the signal without clipping, ensuring linear behavior.

## 2.D.

 
### 1. Plot of $V_o$ and $V_s$ for the case of $A_o = 10^6$



### 2. Spice Netlist for the case of $A_o = 10^6$

```
Rf V0 N001 99000
Ri 0 N001 11000
X$U1 Vs N001 Vcc Vee V0 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m Rail=0
Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vcc Vcc 0 100
Vee 0 Vee 100
V1 Vs 0 1
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```
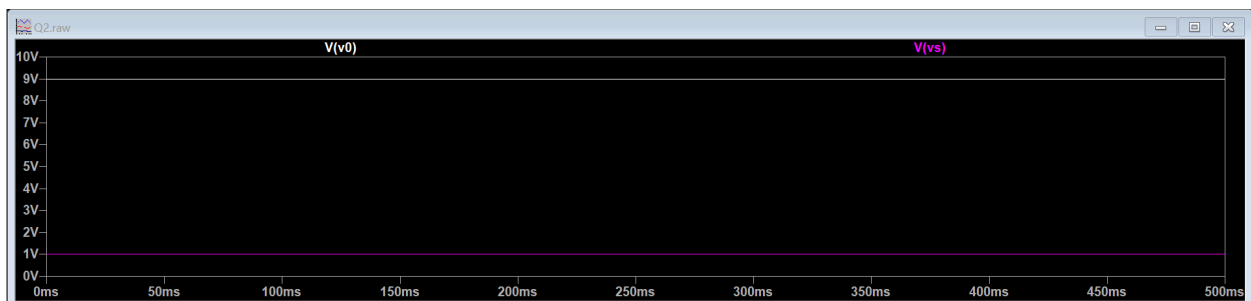
### 3. Plot of $V_o$ and $V_s$ for the case of $A_o = 100$



**4. Netlist for the case of  $A_o = 100$**

```
* C:\Users\Josh\Documents\COMPENG\Y2S2\2CF3\Assignment1\Q2.asc
Rf V0 N001 99000
Ri 0 N001 11000
X$U1 Vs N001 Vcc Vee V0 level2 Avol=100 GBW=10Meg Slew=10Meg Ilimit=25m Rail=0
Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vcc Vcc 0 100
Vee 0 Vee 100
V1 Vs 0 1
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

**5. State the simulated circuit gain in the case when  $A_o = 100$ .**

Observed gain = 9

**6. State the gain error in percentage compared to the ideal gain of 10.**

Percent difference =  $(\text{observed} - \text{true})/\text{true} = (9-10)/10 = 10\%$